

AP Phys 2 Unit 3.C.2 Notes - Resistance & Resistor Circuits

3.C.2 Resistance and Resistor Circuits



Resistance: Units = Ohms (Ω)

Resistance: opposition to current.



Unit analysis (from Ohm's Law):

$$R = \frac{V}{I} = \frac{\frac{J}{C}}{\frac{C}{s}} = \frac{J \cdot s}{C^2} = \frac{\frac{kg \cdot m^2}{s^2} \cdot s}{C^2} = \frac{\frac{kg \cdot m^2}{s}}{C^2} = \frac{kg \cdot m^2}{C^2 \cdot s}$$

Resistance is Futile!


Resistance Factors

Type of material (resistivity),

length (proportional:
longer = greater resistance),

area (inversely proportional:
larger area = lower resistance),

temperature (proportional).

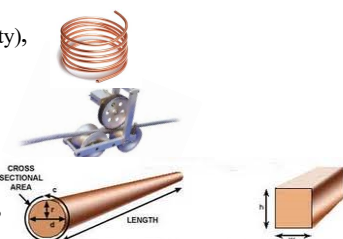

$R = \frac{\rho \ell}{A}$	ρ = resistivity of material ($\Omega \cdot m$) (Resources P. 5) ℓ = length of material (m) A = cross sectional area (m^2)
---------------------------	--

AP Equation

Thermal Effects

As materials heat up, their resistivity (and therefore resistance) increases. (Remember the light bulb lab?)

Calculate the new resistivity of your substance using:

$\rho = \rho_0 (1 + \alpha \Delta T)$	ρ_0 = resistivity at $20^\circ C$ α = coefficient of resistivity (P. 5) T = temperature difference ($^\circ C$)
---------------------------------------	---

Because resistivity and resistance are directly related:

$R = R_0 (1 + \alpha \Delta T)$	R_0 = resistance at $20^\circ C$ α = coefficient of resistivity (P. 5) T = temperature difference ($^\circ C$)
---------------------------------	---

1. Resistivity Example

What is the resistance of a tungsten filament at $1500^\circ C$ if its resistance is 9.5Ω at $20^\circ C$?

$$\begin{aligned}
 R &= R_0 (1 + \alpha \Delta T) \\
 &= 9.5 \Omega (1 + 4.5 \times 10^{-3} / ^\circ C \cdot (1500^\circ C - 20^\circ C)) \\
 &= 73 \Omega
 \end{aligned}$$


Resistor Codes

Resistors have a printed resistance that at-a-glance tells what its resistance value is (see Resources 5).

The first and second bands (read from closest band end of resistor) are two numbers.

The third band is a multiplier.


The fourth is a +/- tolerance band.

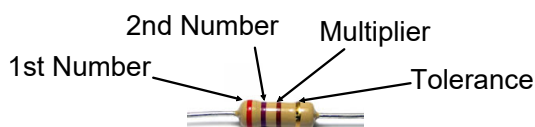


AP Phys 2 Unit 3.C.2 Notes - Resistance & Resistor Circuits

2. Resistor Code Example


What are the values of the following resistors?

A.  10 megaohms +/- 500 kohms

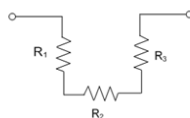
B.  360 ohms +/- 18 ohms

Resistor Circuits

Resistors can be arranged in series or parallel:



Series: current has only one path

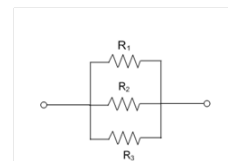


Parallel: current has multiple possible paths

Calculating Series Resistance

Series resistance (R_s) calculation:

$$R_s = R_1 + R_2 + R_3 \dots$$

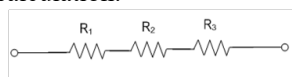

$$R_s = \sum_i R_i$$

AP Equation


R = Resistance
i = individual

Resistance is additive - current travels through more obstacles (like little football players).

Analogous to parallel capacitor circuit.

3. Series Example

What is the resistance?

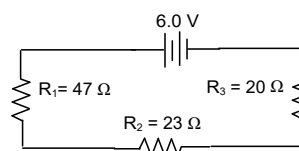

$$R_s = R_1 + R_2 + R_3 + \dots$$

$$R_s = 47\Omega + 23\Omega + 20\Omega = 90\Omega$$


Calculating Parallel Resistance

Parallel resistance (R_p):

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Or:
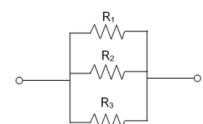
$$R_p = \left(R_1^{-1} + R_2^{-1} + R_3^{-1} \dots \right)^{-1}$$



$$\frac{1}{R_p} = \sum_i \frac{1}{R_i}$$

AP Equation

R = Resistance
i = individual


There are more paths for current to follow, so R_p is always less than the lowest resistor.

Analogous to serial capacitors.

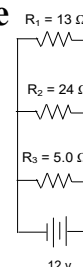4. Parallel Example

Calculate the resistance:


$$\begin{aligned} R_p &= \left(R_1^{-1} + R_2^{-1} + R_3^{-1} \dots \right)^{-1} \\ &= \left(13\Omega^{-1} + 24\Omega^{-1} + 5.0\Omega^{-1} \right)^{-1} \\ &= 3.14\Omega \end{aligned}$$



AP Phys 2 Unit 3.C.2 Notes - Resistance & Resistor Circuits


Mixed Circuits: Series & Parallel

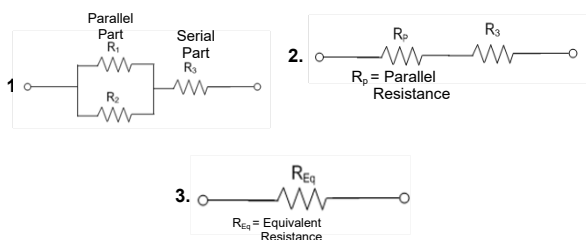Sequentially reduce series/parallel sections until total resistance reduces to one equivalent resistance (R_{eq}).




5. Mixed Example

What is the equivalent resistance?

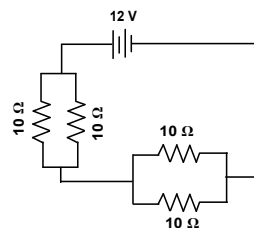

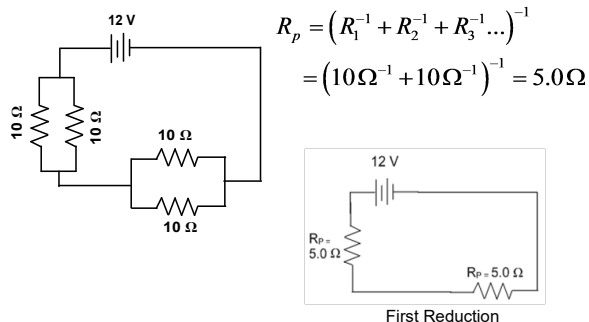5. Mixed Example


First, solve the two parallel portions of the circuit.



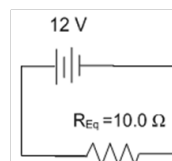5. Mixed Example

Finally, compute equivalent resistance (it is now effectively a series circuit).

$$R_{eq} = 5.0\Omega + 10.0\Omega = 15.0\Omega$$



A Note On Grounding


Some circuits use a ground to save on wiring.

Symbol:

When an object is grounded, it has an electrical path available that has extremely low resistance.

Vehicles: a chassis ground allows current to flow through the frame, and return to the battery.

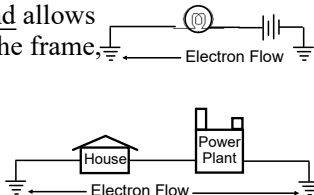Homes: an earth ground allows current to flow between a home and the power plant.



Homework

3.C.2 Problems.
Due: Next Class.