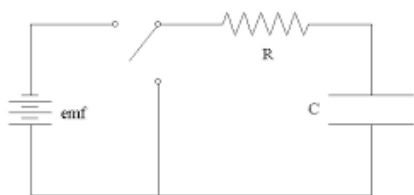


## AP Phys 2 Unit 3.C.5 Notes - RC Circuits

### 3.C.5 - Resistor/Capacitor (RC) Circuits



### Quick Capacitor Review

Capacitors store charge and electrical energy:

$$U_c = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2} \frac{Q^2}{C}$$

AP Equations

Non-AP Equation


$U_c$  = Energy (J)  
 $Q$  = Charge (C)  
 $V$  = Voltage (Volts: J/C)  
 $C$  = Capacitance (Farads: C/V)

### Resistor/Capacitor (RC) Circuits

Note: RC is NOT 'remote control'.

A battery charges a capacitor, and a serial resistor moderates current.

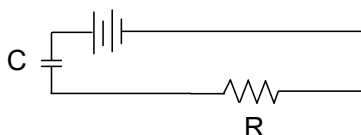The larger the resistor, the longer it takes to charge the capacitor.



### Time Constant = $\tau$

It takes an infinite time for full charge: charges accumulating on capacitor repel additional charges.

BUT: a usable charge takes a short time.

For calculations, a time constant ( $\tau$ ) of charging is:

$$\tau = RC$$

$R$  = Resistance (Ohms)  
 $C$  = Capacitance (Farads)

Units are in seconds.

Unit Analysis:

$$R \cdot C = \frac{V}{I} \cdot \frac{C}{V} = \frac{C}{I} = \frac{C}{\frac{C}{s}} = s$$

### Charging Capacitors: Voltage

During charging, voltage increases logarithmically.

Eventually, capacitor and battery voltage equalize; until then, capacitor voltage is:


$$V_C = V_0 [1 - e^{-t/\tau}]$$

$V_C$  = Capacitor Voltage  
 $V_0$  = Battery Voltage  
 $t$  = time (s)  
 $\tau$  = time constant (s)


Note:  $e$  is the base of *natural logarithms*. It approximately equals 2.718; is common in science.
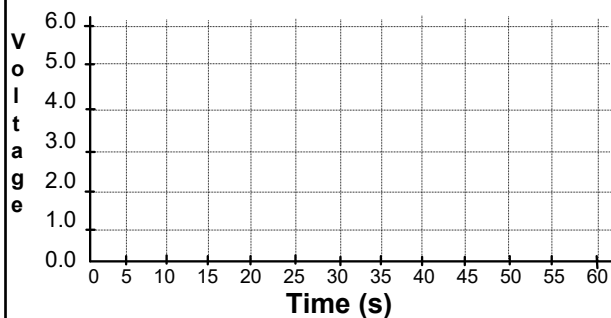
### 1. Capacitor Charging Demo.

I will charge the capacitor, and shout out numbers every five seconds. Please write them for a graph.



## Charging Capacitors: Voltage Graph

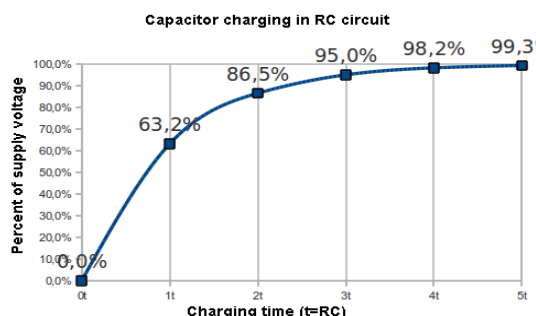

This graph shows amount of voltage across a capacitor at different time constants.

## Manipulating Logarithms.

Crash course in logarithms (to isolate t or τ):

If  $e$  is raised to a power, take the natural log of both sides:

$$e^{-t/\tau} = 0.26$$

$$\ln(e^{-t/\tau}) = \ln(0.26)$$

$$-t / \tau = -1.35$$

Use calculator's ln button.

Rabbit hole to next slide!

## Why 63.2%?

Substituting  $\tau$  for  $t$  in the voltage equation, gives:

$$V_C = V_0[1 - e^{-t/\tau}]$$


$$V_C = V_0[1 - e^{-\tau/\tau}] = V_0[1 - e^{-1}] = V_0[1 - \frac{1}{2.718}]$$

$$V_C = 0.632V_0$$

A capacitor is "fully charged" after "several time constants."
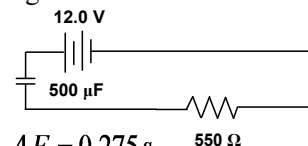
## 2. Voltage Example

What will capacitor voltage be after 0.150 seconds?



$$\tau = RC = 550\Omega \cdot 5.00 \times 10^{-4}F = 0.275s$$

$$V_C = V_0[1 - e^{-t/\tau}]$$

$$= 12.0V[1 - e^{-0.15s/0.275s}]$$


$$= 5.05V$$

## 3. Energy Example

How much energy does the capacitor store after it has charged for 85 seconds?

Find time constant:
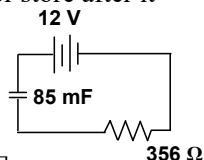
$$\tau = RC = 356\Omega \cdot 85mF = 30.3s$$



Then voltage:

$$V_C = V_0[1 - e^{-t/\tau}] = 12V \left[ 1 - e^{-\frac{85.0s}{30.3s}} \right] = 11.3V$$

Finally:

$$U_C = \frac{1}{2}C(\Delta V)^2 = \frac{1}{2} \cdot 0.085F \cdot (11.3V)^2 = 5.43J$$

## Discharging Capacitors Through Resistors

As a capacitor discharges through a resistor, voltage diminishes logarithmically:

$$V_C = V_0 e^{-t/\tau}$$


$V_C$  = Capacitor Voltage  
 $V_0$  = Battery Voltage  
 $t$  = time (s)  
 $\tau$  = RC (s)

## AP Phys 2 Unit 3.C.5 Notes - RC Circuits
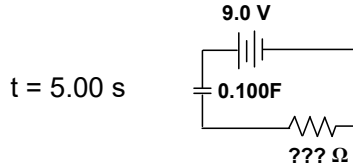
### 4. Flashy Example

A flash camera uses a 9.0 volt battery to charge a 0.100 F capacitor through a resistor  
(Ever heard that high pitched sound from a camera? That's the sound of a capacitor charging!).

What is the resistance if the capacitor needs 80% of max. voltage in 5.00 seconds?



### Flashy Answer

First, 80% of maximum voltage is 7.2 V.

Next:  $V_C = V_0[1 - e^{-t/\tau}]$

$$7.2V = 9.0V[1 - e^{-5.00/\tau}]$$

$$\frac{7.2V}{9.0V} - 1 = -e^{-5.00/\tau}$$

$$0.2 = e^{-5.00/\tau}$$


$$\ln(0.2) = \ln(e^{-5.00/\tau})$$

$$-1.609 = -5.00 / \tau$$

So:  $\tau = 3.11 \text{ s}$

Finally:  $\tau = RC = 3.11 \text{ s}$
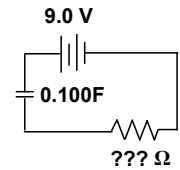
$$R = \frac{3.11 \text{ s}}{0.100 \text{ F}} = 31.1 \Omega$$



### Homework

3.C.5 Problems.  
Due: Next Class.

Finish Unit 3.C Review Problems  
Due: ???